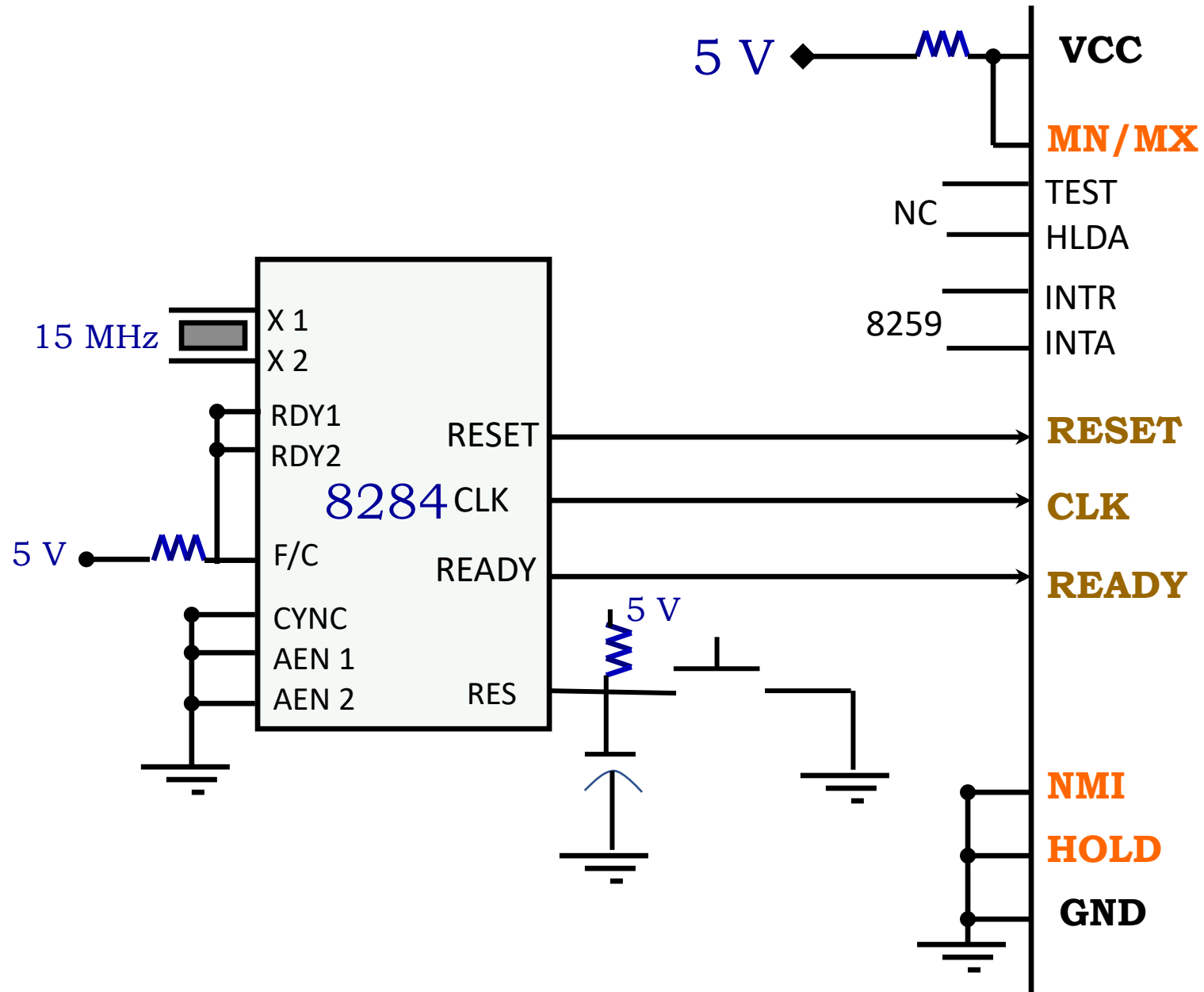



GROUP-12

HARDWARE DESIGN


8086 Inputs





System Bus of 8086 (Address)

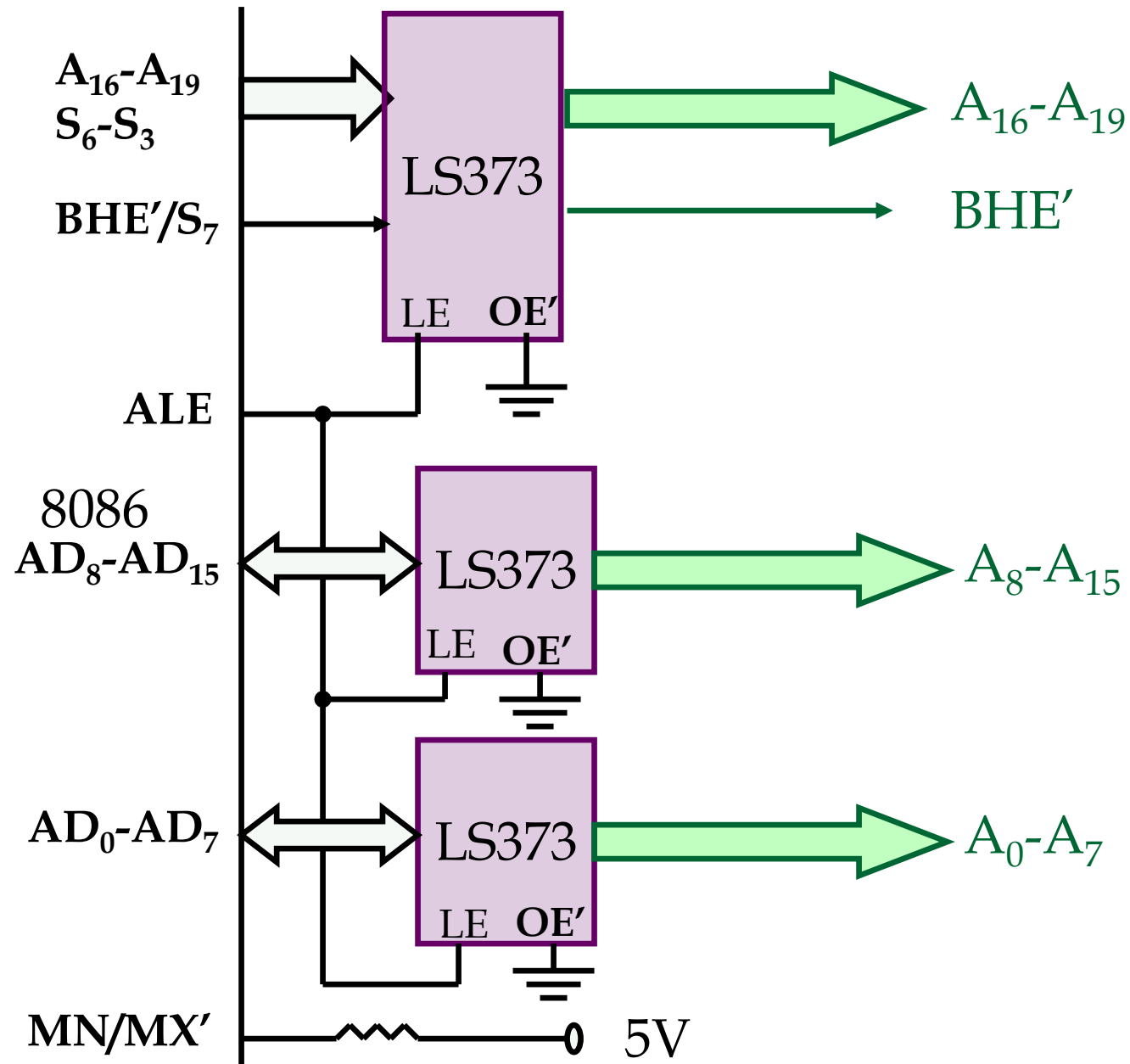



System Bus of 8086(Data + Control)

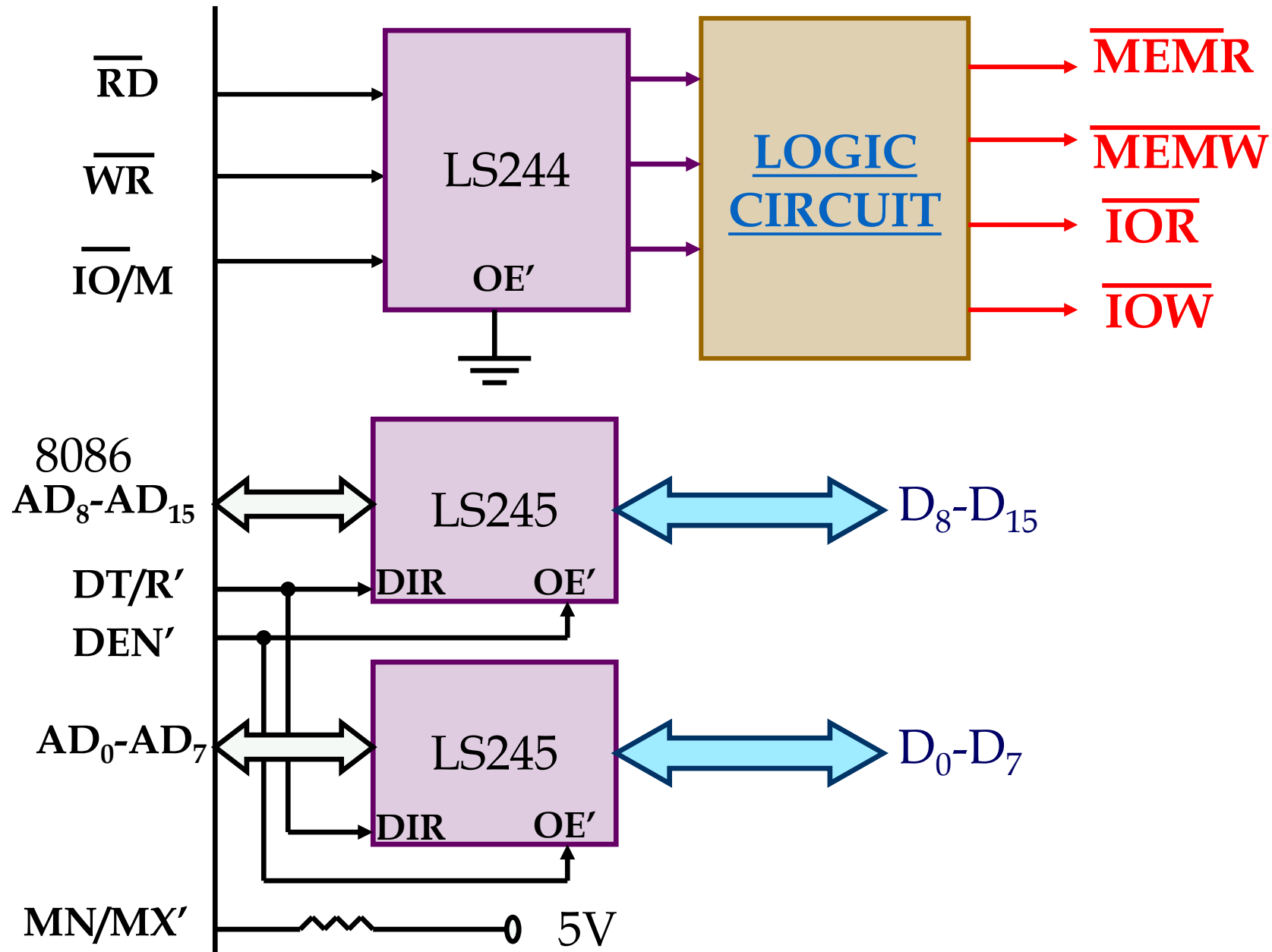


Memory & I/O Decoding

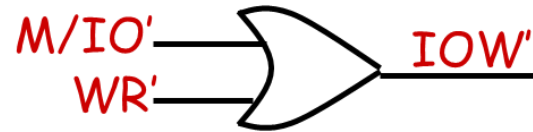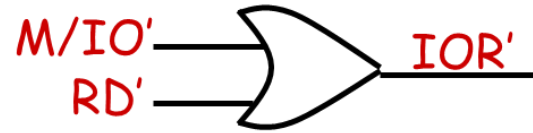

M/IO'	RD'	WR'	Bus cycle
1	0	1	$MEMR'$
1	1	0	$MEMW'$
0	0	1	IOR'
0	1	0	IOW'



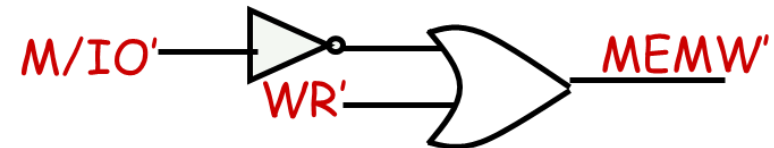
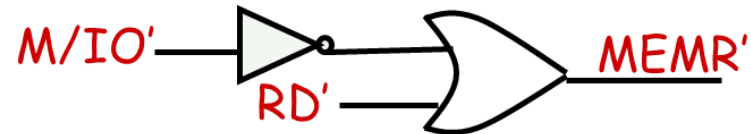


Memory Decoding

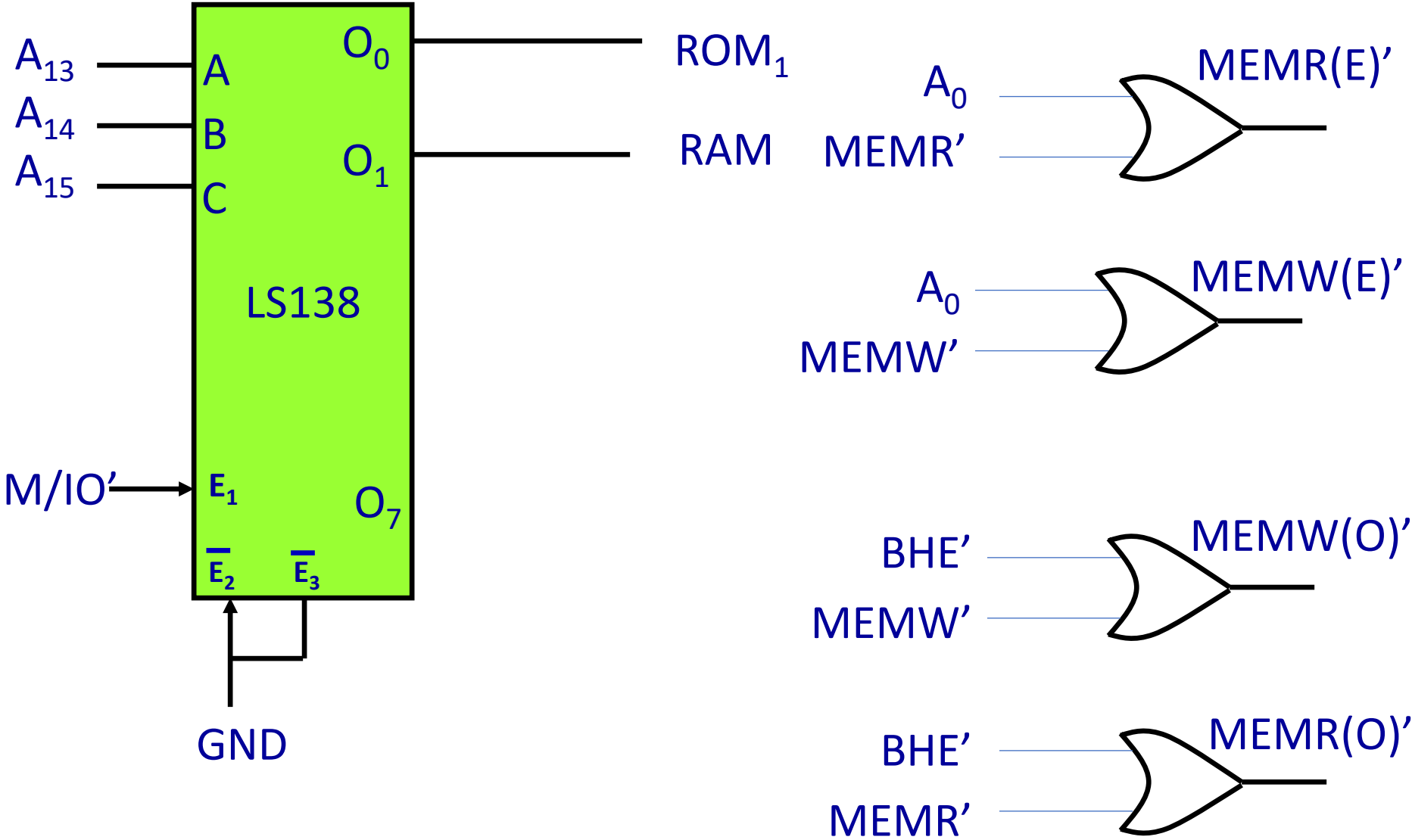


Memory Decoder

Memory Interfacing

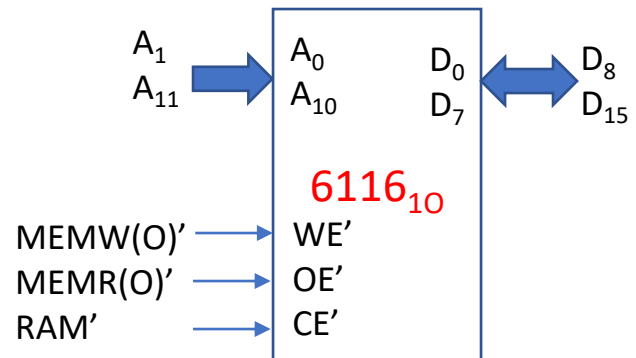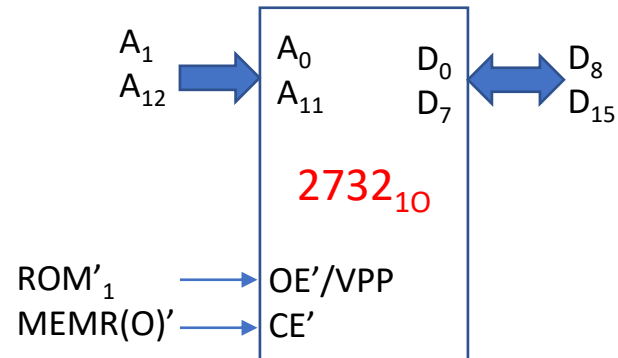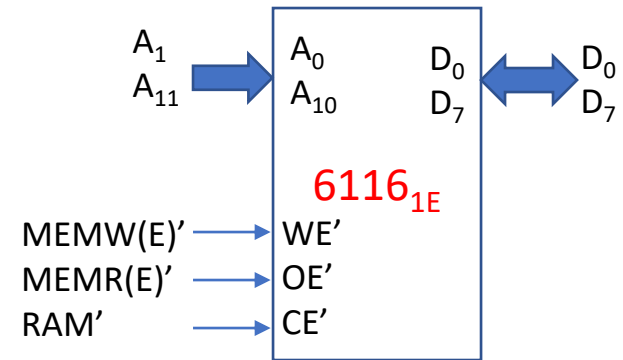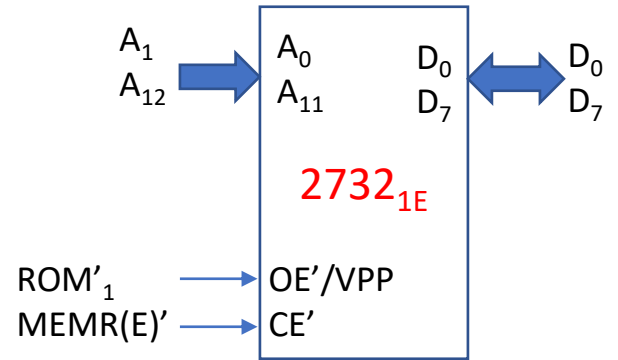


I/O Decoding

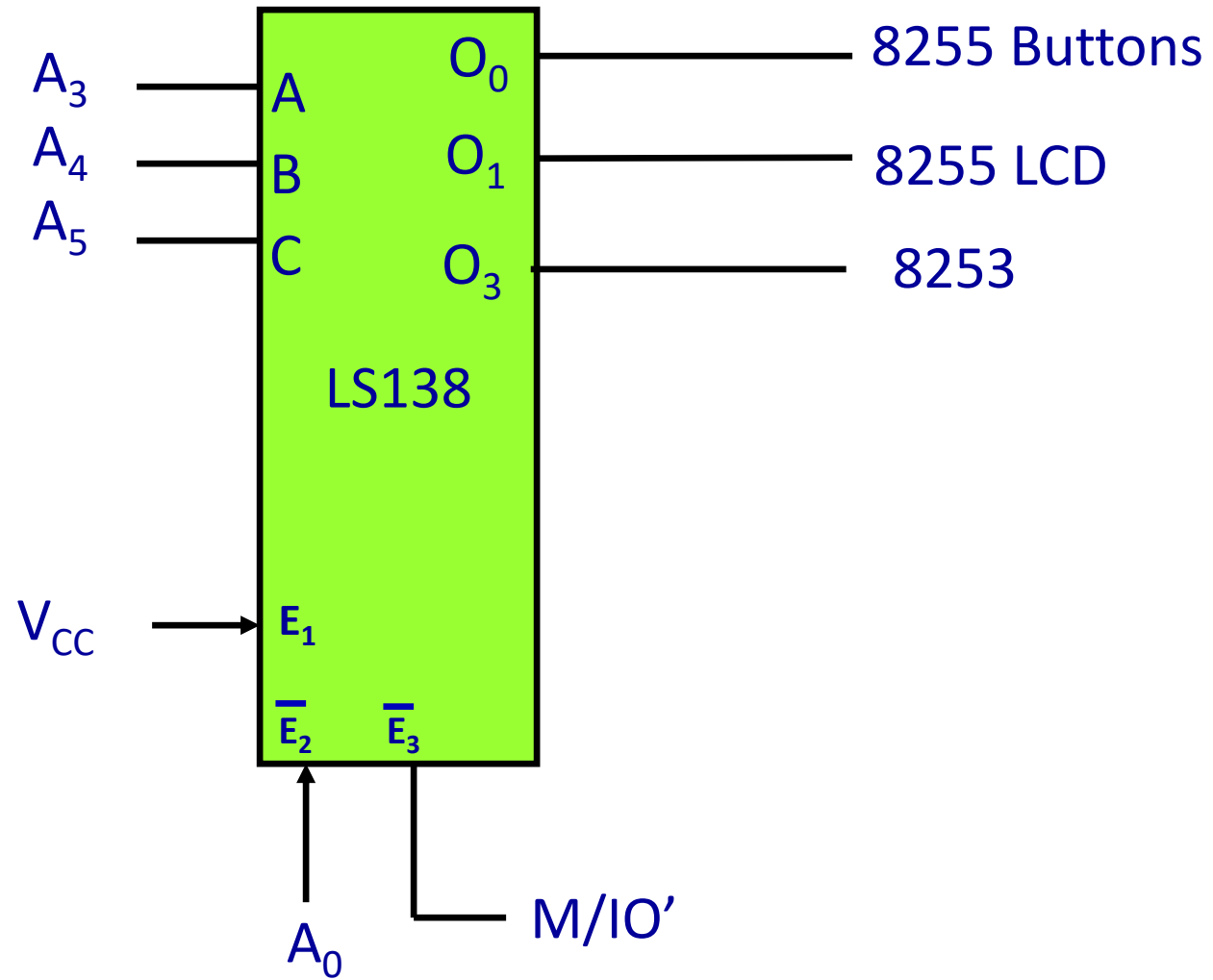

I/O Decoder

8255 Interface to the processor(Keypad)

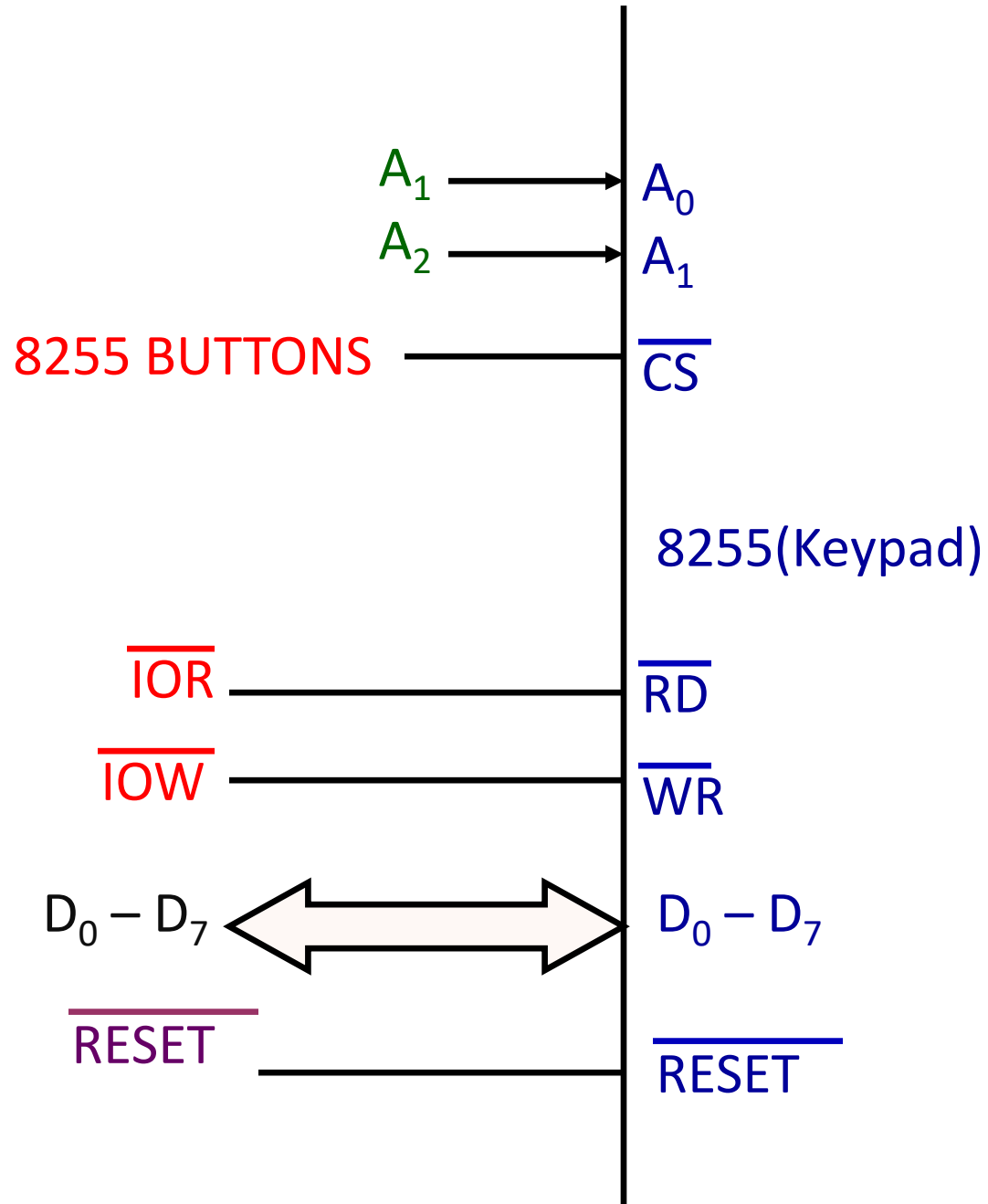



Push Button

Keyboard Interfacing(Port A)

PA0	PA1	PA2	PA3	PA4	PA5	PA6	PA7	HEX VALUE	BUTTON
1	1	1	1	1	1	1	0	FE _H	0
1	1	1	1	1	1	0	1	FD _H	1
1	1	1	1	1	0	1	1	FB _H	2
1	1	1	1	0	1	1	1	F7 _H	3
1	1	1	0	1	1	1	1	EF _H	4
1	1	0	1	1	1	1	1	DF _H	5
1	0	1	1	1	1	1	1	BF _H	6
0	1	1	1	1	1	1	1	7F _H	7


Keyboard Interfacing(Port B)

PB0	PB1	PB2	PB3	PB4	PB5	PB6	PB7	HEX VALUE	BUTTON
1	1	1	1	1	1	1	0	FE _H	8
1	1	1	1	1	1	0	1	FD _H	9
1	1	1	1	1	0	1	1	FB _H	Y
1	1	1	1	0	1	1	1	F7 _H	N
1	1	1	0	1	1	1	1	EF _H	Enter
1	1	0	1	1	1	1	1	DF _H	Backspace
1	0	1	1	1	1	1	1	BF _H	Cancel
0	1	1	1	1	1	1	1	7F _H	Item Code


Keyboard Interfacing(Port C)

PC0	PC1	PC2	PC3	PC4	PC5	PC6	PC7	HEX VALUE	BUTTON
1	1	1	1	1	1	1	0	FE _H	Quantity
1	1	1	1	1	1	0	1	FD _H	Total
1	1	1	1	1	0	1	1	FB _H	Mode
1	1	1	1	0	1	1	1	F7 _H	Trans
1	1	1	0	1	1	1	1	EF _H	Program
1	1	0	1	1	1	1	1	DF _H	Add Item
1	0	1	1	1	1	1	1	BF _H	Del Item
0	1	1	1	1	1	1	1	7F _H	Cost


8255 INTERFACE(FOR LCD)

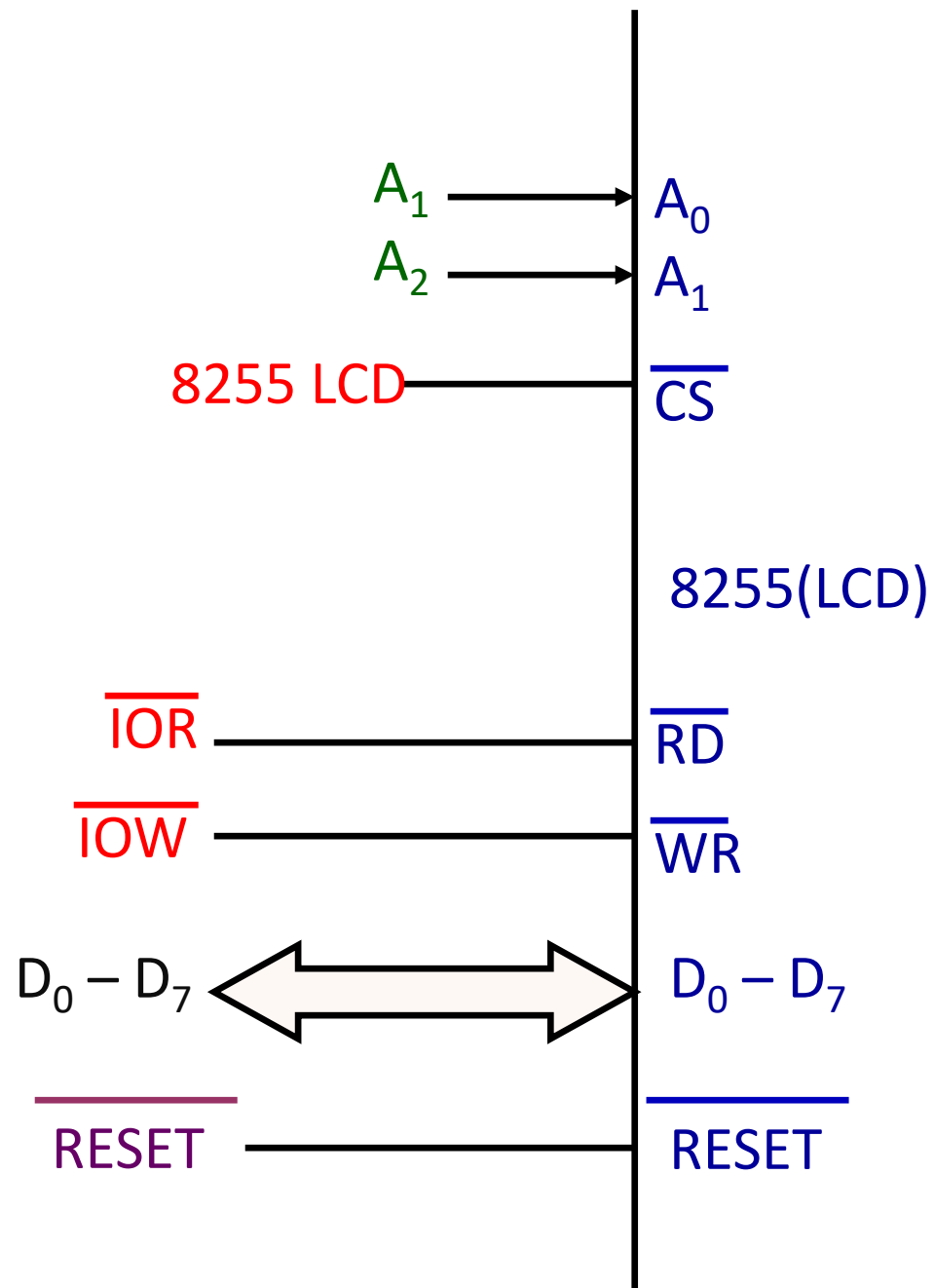


LCD Interfacing

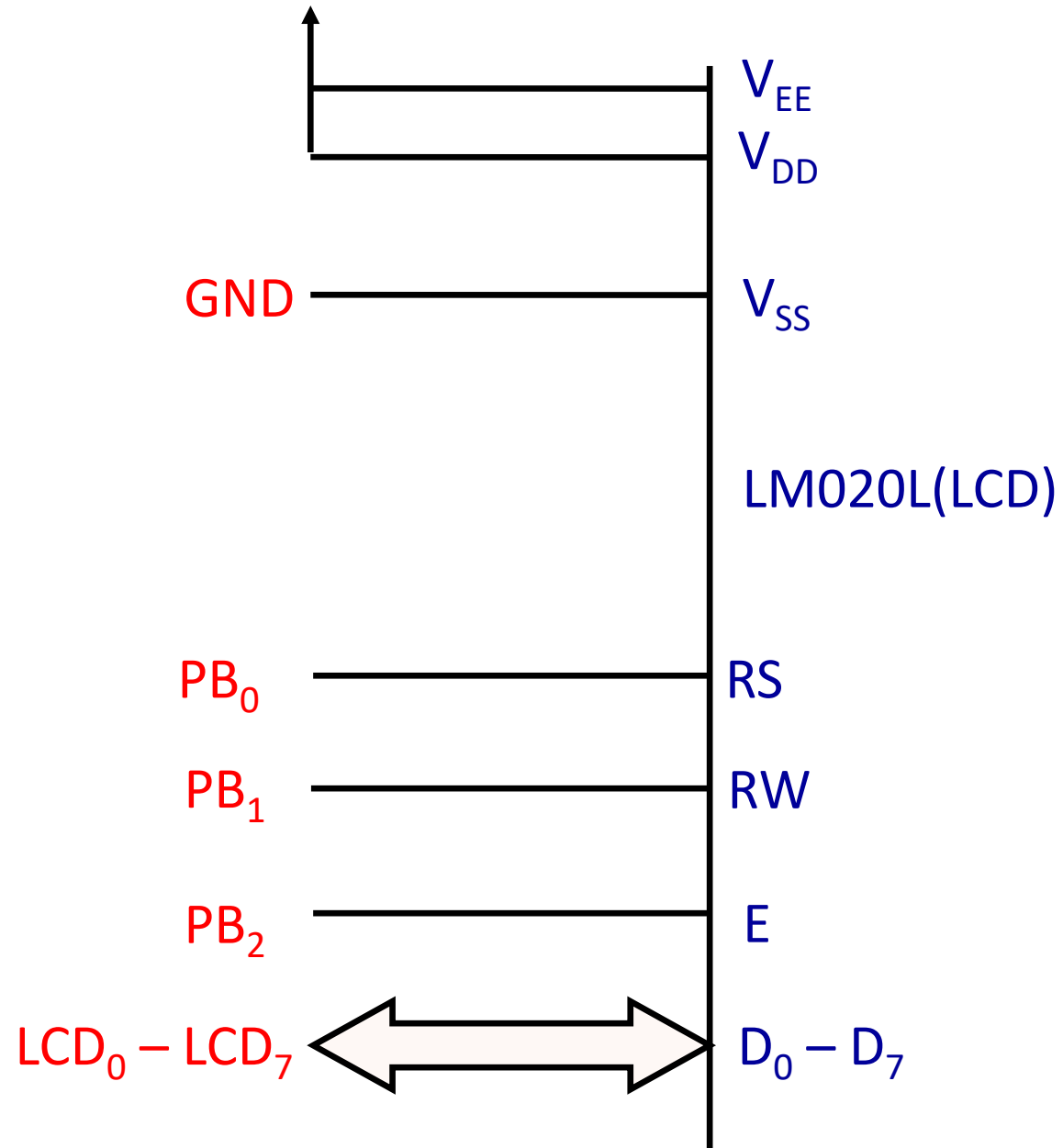

Buffer for LCD Interfacing

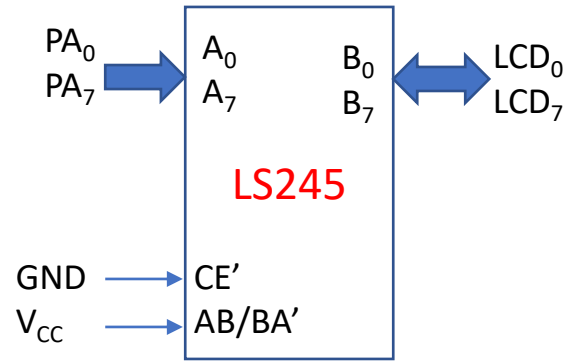



Buffer for PA[0..7]

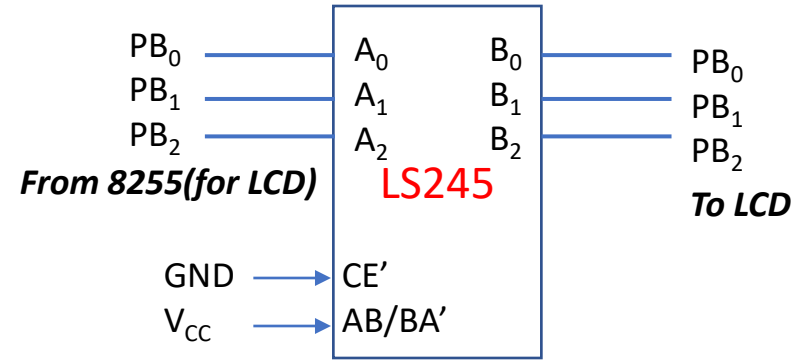


Buffer for PB[0..2]

8253 Interfacing

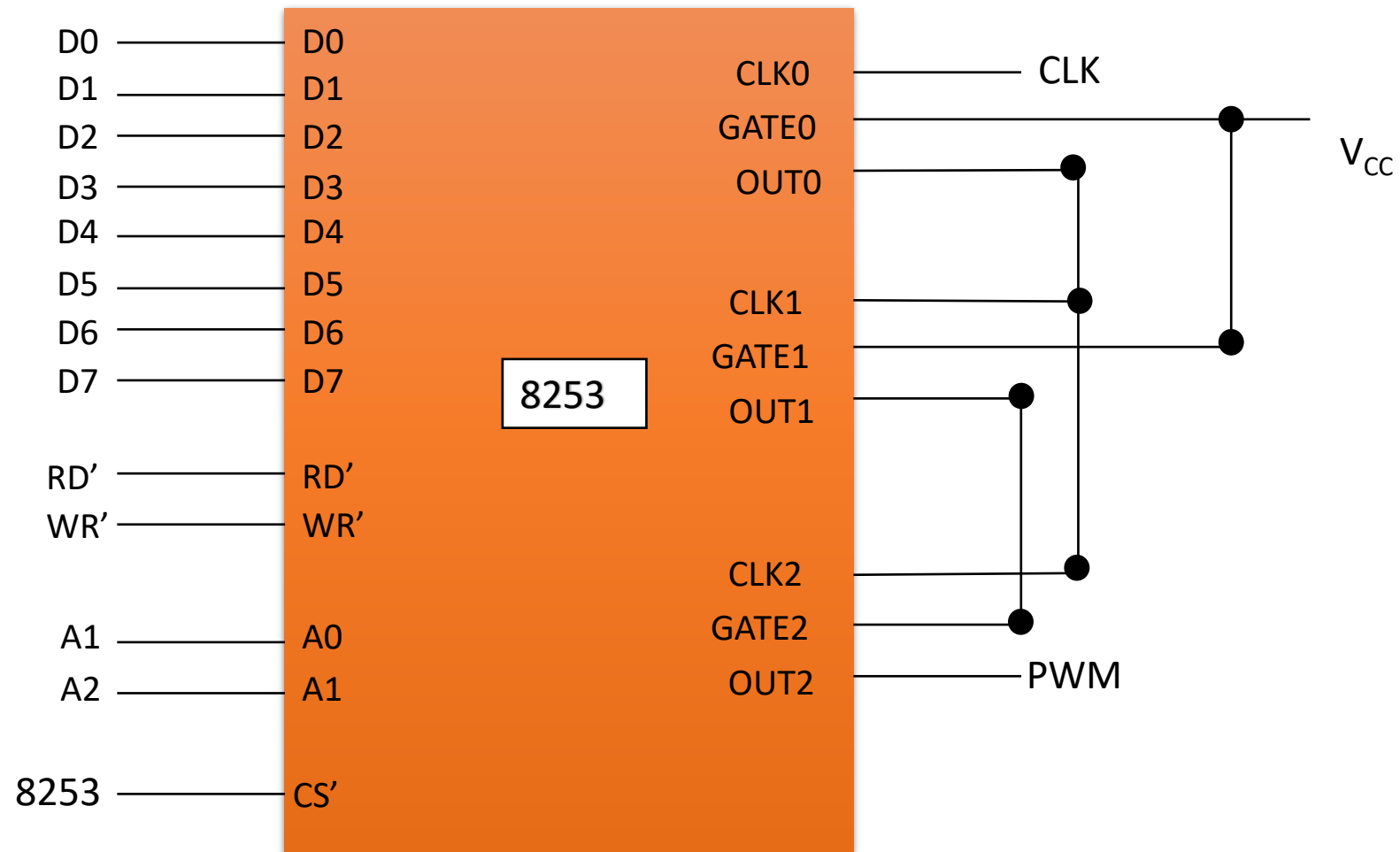

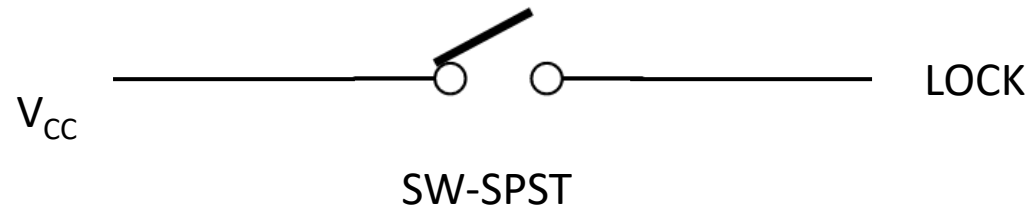

LOCK

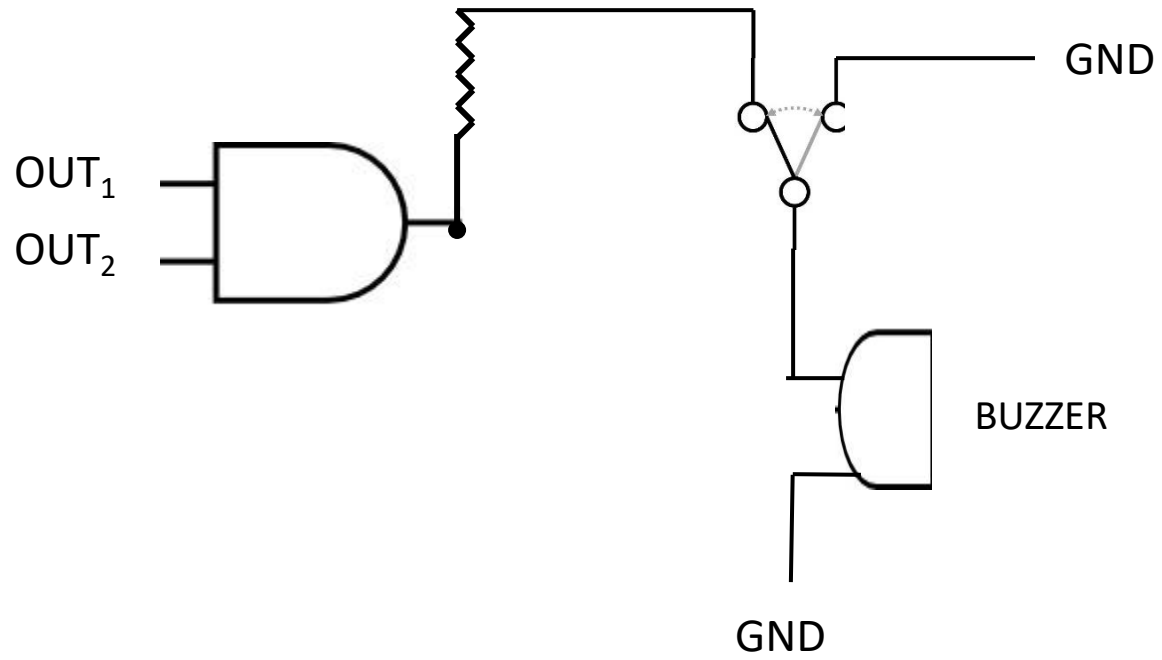

BUZZER